

ESC201A EndSem Part 3

RAGHAV SHUKLA

TOTAL POINTS

10 / 20

QUESTION 1

Q1 10 pts

1.1 1(a) 1 / 2

+ 2 pts Completely Correct

✓ + 0 pts *Completely Incorrect*

+ 0 pts Not Attempted

+ 0 pts Copied

+ 1 Point adjustment

1.2 1(b) 3 / 3

+ 3 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

✓ + 1 pts *Correct number of 1 to 2 decoders used*

✓ + 2 pts *Final implementation correct*

1.3 1(c) 4 / 5

+ 5 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

✓ + 2 pts *Minimized PoS expression correct*

+ 3 pts Final implementation using 2-input NOR gates correct

+ 2 Point adjustment

QUESTION 2

Q2 10 pts

2.1 2(a) 2 / 4

+ 4 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

✓ + 2 pts *Excitation table correct*

+ 2 pts Final implementation correct

2.2 2(b) 0 / 6

+ 6 pts Completely Correct

+ 0 pts Completely Incorrect

✓ + 0 pts *Not Attempted*

+ 0 pts Copied

+ 1 pts Counter states and transitions correctly identified

+ 3 pts Assignment to D inputs of the two flip flops correct

+ 2 pts Final implementation schematic correct

Name

RAGHAV SHUKLA

Roll No.

210800

Seat/Room No.


260 / L19

1 (a). Prove using basic postulates of Boolean algebra that $x + x \cdot y = x + y$. [2]


$$\begin{aligned}
 \text{R.H.S.} &= x + y = (x + y) \cdot (x + \bar{x}) \quad [\because x + \bar{x} = 1 \text{ and } (x + y) \cdot 1 = x + y] \\
 &= x \cdot x + x \cdot \bar{x} + y \cdot x + y \cdot \bar{x} \quad (\text{Distributivity over multiplication}) \\
 &= x \cdot x + (x \cdot \bar{x} + x \cdot y) + (y \cdot x + y \cdot \bar{x}) \\
 &= x \cdot x + x(x + \bar{x}) + x(y) + y \cdot \bar{x} \quad (x \cdot x = x, 1 + y = 1) \\
 &= x + x + x + y \cdot \bar{x} = x + y \cdot \bar{x} = \text{L.H.S.}
 \end{aligned}$$

Also, $p + q = (p + q)(p + q)$

1 (b). Implement a 3 to 8 decoder using only 1 to 2 decoders. Assume that each decoder has an enable signal. Label all the input and output lines. [3]

 
Standard Decoder \equiv 

 1 (c). Determine the minimized product of Sum (PoS) expression for the K-map shown below and implement using only 2-input NOR gates. Assume that complements of input variables are also available and need not be generated using gates. [5]



		$x_3 x_4$			
		00	01	11	10
$x_1 x_2$	00	1	1	1	0
	01	0	1	0	0
	11	0	0	0	0
	10	1	0	1	0

 Minimized POS expression = $(\bar{x}_2 + \bar{x}_4) \cdot (\bar{x}_3 + \bar{x}_4) \cdot (\bar{x}_3 + \bar{x}_2) \cdot (\bar{x}_1 + \bar{x}_3 + \bar{x}_4)$
 A POS This POS expression corresponds to a OR-AND network.



The above diagram is obtained after cancellation 2 successive NOT gates wherever encountered.

2(a). For the Flip-flop with two inputs A and B whose characteristic table is shown below, determine first the excitation table and then implement the flip-flop using a D flip-flop and a 4 to 1 multiplexer. [4]

Excitation table


$Q(t)$	$Q(t+1)$	$A \cdot B$	D
0	0	1 X	0
0	1	0 X	1
1	0	0 1 or 1 0	0
1	1	0 0 or 1 1	1

A	B	$Q(t+1)$	State
0	0	1	Set
0	1	$\overline{Q}(t)$	Toggle
1	0	0	Reset
1	1	$Q(t)$	Hold

We want $D = f(A, B, Q)$

observe that when $Q = 0$, $D = \overline{A}$

 $Q = 1$, $D = A \cdot B + \overline{A} \cdot \overline{B} = A \odot B$



2(b). Design a synchronous circuit using D flip-flops that can produce the outputs y_0 and y_1 from a clock input X as shown below. The output sequence repeats after the dotted line shown below. [6]

