

ESC201A EndSem Part 2

RAGHAV SHUKLA

TOTAL POINTS

10.5 / 19

QUESTION 1

Q1 9 pts

1.1 1(a) 1 / 3

- + 3 pts Completely Correct
- + 0 pts Completely Incorrect
- + 0 pts Not Attempted
- + 0 pts Copied
- ✓ + 1 pts DC Equivalent circuit correctly found
- + 1 pts Transistor currents correctly found
- + 1 pts Collector voltage correctly found

1.2 1(b) 0.5 / 6

- + 6 pts Completely Correct
- + 0 pts Completely Incorrect
- + 0 pts Not Attempted
- + 0 pts Copied
- + 3 pts Transistor currents correctly found
- + 1.5 pts RE correctly calculated
- + 1.5 pts R2 correctly calculated
- + 0.5 Point adjustment

QUESTION 2

Q2 10 pts

2.1 2(a) 5 / 6

- + 6 pts Completely Correct
- + 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 2 pts Desirable circuit schematic correctly drawn

✓ + 1 pts Feedback resistance correctly found

✓ + 1.5 pts Resistors corresponding to source v1 correctly found

✓ + 1.5 pts Resistors corresponding to source v2 correctly found

+ 1 Point adjustment

2.2 2(b) 4 / 4

✓ + 4 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 1 pts Bias state of diodes correctly found

+ 1.5 pts Vo1 correctly found

+ 1.5 pts Vo2 correctly found

Name **RAGHAV SHUKLA**

Roll No.


210800

Seat/Room No.

260 / L19

1 (a). Carry out dc analysis to determine collector voltage for the circuit shown below. Assume that current gain $\beta_F = 100$. [3]

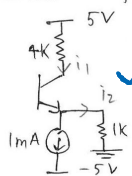
In DC analysis, we turn off all AC sources and treat capacitors as opens. We obtain the following circuit -



$$5 - (4 \times 10^3) i_1 = -V_{CE}$$


$$-10^3 i_2 = 0$$

$$i_2 + 10^{-3} = i_1$$

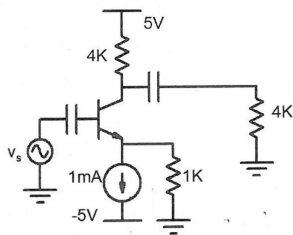

1 (b). Determine suitable values for resistances R_E and R_2 so as to obtain a voltage gain of for the amplifier shown. Assume that dc value of base voltage is 5.9V, transistor is in forward active mode, thermal voltage $V_T = 0.026V$ and $\beta_F = 100$. [6]


DC Analysis

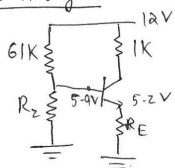

$$I_E = \frac{5.2V}{R_E}$$

$$I_B = \left(\frac{12-5.9}{61K} \right) - \left(\frac{5.9}{R_2} \right)$$
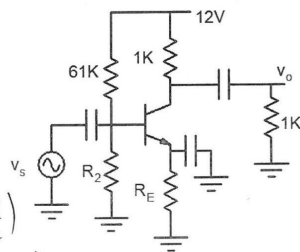
$$I_C = 100 \left(\left(\frac{6.1}{61K} \right) - \left(\frac{5.9}{R_2} \right) \right)$$




$$\text{We get } I_C + I_B = I_E \Rightarrow 100 \left(0.1 - \frac{5.9}{R_2} \right) = \frac{5.2}{R_E}$$

$$R_2 \text{ \& } R_E \rightarrow k\Omega$$

In AC analysis, we use small signal model, $r_{\pi} = \frac{\beta}{g_m}$

$$g_m = \frac{I_C}{V_T} \checkmark$$

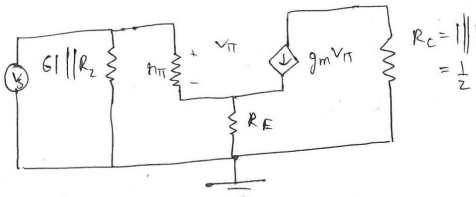

$$\text{We find } A_v = \frac{+g_m R_C}{1 + g_m \left(1 + \frac{1}{\beta} \right) R_E} = +50$$

$$\Rightarrow g_m = 100 \left(1 + g_m \left(1 + \frac{1}{100} \right) R_E \right)$$

$$\Rightarrow \boxed{g_m = 100 + 101 g_m R_E}$$

$$g_m = \frac{I_C}{V_T} = 100 \left(0.1 - \frac{5.9}{R_2} \right) \times \frac{1}{0.026}$$

$$\Rightarrow 100 \left(0.1 - \frac{5.9}{R_2} \right) \times \frac{1}{0.026} = 100 + 101 \times 100 \left(0.1 - \frac{5.9}{R_2} \right) \times \frac{R_E}{0.026}$$

$$\Rightarrow \left(\frac{5.2}{R_E} \right) \times \frac{1}{0.026} \times \frac{1}{101} = 1 + 101 \times \left(\frac{5.2}{R_E} \right) \times \frac{1}{101} \times \frac{R_E}{0.026}$$


$$\Rightarrow \frac{5.2 \times 1}{R_E} \times \frac{200}{101 R_E} = 1 + 200 \Rightarrow R_E = \frac{200}{101 \times 200.1}$$

$$= 9.8517 \times 10^{-3} k\Omega$$

X

2(a). Design an opamp circuit that would produce the output voltage $V_o = -2 \times 10^3 I_1 - 2v_1 + v_2$, where I_1 , v_1 and v_2 are input current and input voltages respectively as shown below. Assume ideal opamp characteristics and use only one opamp. [6]

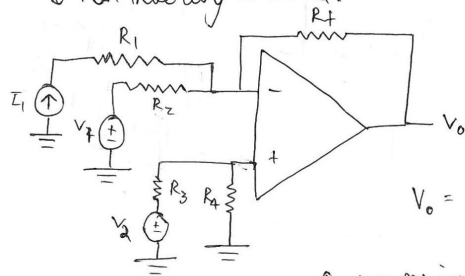Since coefficients of I_1 and v_1 are negative, they will be connected to inverting terminal. v_2 will be connected to non-inverting terminal.



V_o can be found by superposition.

$$V_o = -R_f I_1 - \left(\frac{R_f}{R_2}\right) v_1 + \left(1 + \frac{R_f}{R_2}\right) \left(\frac{R_4}{R_3 + R_4}\right) v_2$$

On comparing with the expression given,

$$R_f = 2 \times 10^3 \Omega = 2k\Omega$$

$$\frac{R_f}{R_2} = 2 \Rightarrow R_2 = 10^3 \Omega = 1k\Omega$$

$$\left(1 + \frac{R_f}{R_2}\right) \left(\frac{R_4}{R_3 + R_4}\right) = 1 \Rightarrow \frac{R_4}{R_3 + R_4} = \frac{1}{3}$$


$$\text{Set } R_4 = 1k\Omega, R_3 = 2k\Omega$$

2(b). Assuming ideal opamp and ideal diodes, determine output voltage V_{o1} and V_{o2} . Note that opamp supply voltages are $\pm 12V$. [4]

Here, the 5V will attempt to force current into circuit. However, the current encounters 2 diodes in reverse bias.

No current will flow through them (open).

The circuit becomes the following

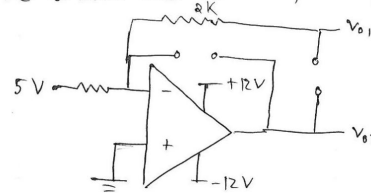

$$\Rightarrow V_{o1} = 5V \text{ (Directly connected)}$$

$$\Rightarrow V_{o2} = -12V$$

The opamp is in open loop mode and goes into saturation (comparator)

