

Experiment 6

Bipolar Junction Transistor (BJT) Circuits: Inverter and Common Emitter Amplifier

Introduction

BJTs are extensively used in all types of electronic circuits. The aim of this part of the experiment is to familiarize you with the basic modes of operation and features of a BJT through the study of simple BJT circuits. The BJT that you will be using in this experiment is BC 547 (the pin diagram is shown in Fig.1), which has a typical current rating of 100 mA (maximum). **Make sure to connect the transistor correctly in the circuits. Also, while changing any component in the circuit, please turn the power supply off, and turn it on again only after all the required changes have been made and the circuit is complete.**

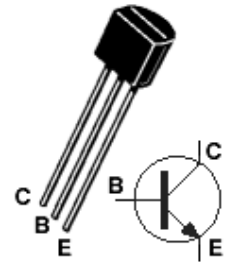




Fig.1

BJT Inverter Circuit

BJT inverter circuit is commonly used to implement the **NOT** function (i.e., the output is an inverted form of the input) using discrete BJTs. The circuit also illustrates the basic modes of operation of a BJT.

Experiment

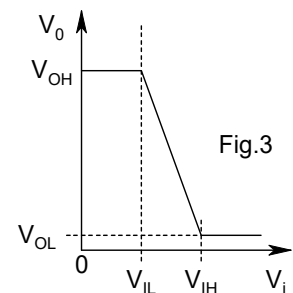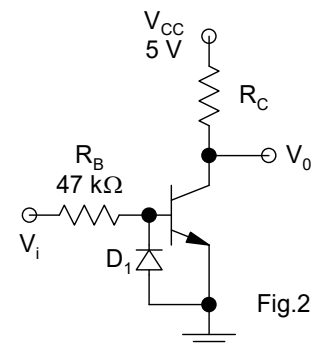- (i) Wire the BJT inverter circuit of Fig. 2. Use $R_C = 1\text{ k}\Omega$.
- (ii) Adjust the FG to obtain a 200 Hz triangular wave (0 to +5 V) and connect the same as the input (V_i) to the circuit.
- (iii) Use the X-Y mode and sketch the voltage transfer characteristic (VTC – V_o versus V_i) of the inverter as seen on the DSO (it should be somewhat similar to the one shown in Fig. 3). Note down the approximate values of V_{OH} , V_{OL} , V_{IL} , and V_{IH} . Indicate the modes of operation of the BJT on the different regions of the VTC.
- (iv) Using the VTC, estimate the current gain β of the transistor.
- (v) Now use $R_C = 15\text{ k}\Omega$, and repeat steps (ii) and (iii).
- (vi) Explain the effect of R_C on the BJT inverter characteristic.



Note: The transistor has a low base-emitter junction reverse breakdown voltage. To ensure that this junction does not break down due to wrong polarity of the applied voltage, the diode D_1 is used - it clamps the maximum reverse bias across the junction to approximately -0.7 V .

Common Emitter Amplifier


BJT amplifiers most commonly employ the common emitter (CE) configuration. You will check the biasing conditions of the given circuit and also test the CE amplifier.

Experiment

Before coming to the lab, you should have analyzed the given BJT circuit (for $R_C = 1.5\text{ k}\Omega$ and $15\text{ k}\Omega$) and calculated the currents I_B , I_C , and I_E , and the voltages V_B , V_C , and V_E . Use $\beta = 100$, $V_{BE} = 0.7\text{ V}$, and $V_{CEsat} = 0.2\text{ V}$.

Common Emitter Amplifier using the BJT Circuit

- (i) Wire the CE amplifier circuit of Fig. 4, omitting the capacitors, R_L , and FG connections. Choose $R_C = 3.3 \text{ k}\Omega$. Make neat connections such that different points of the circuit are easily accessible.
- (ii) Measure the node voltages V_B , V_C , and V_E using the DMM.
- (iii) Estimate I_B , I_C , and I_E . Tabulate the theoretical and the measured results (Table 1).
- (iv) What is the mode of operation of the BJT? Justify your answer.

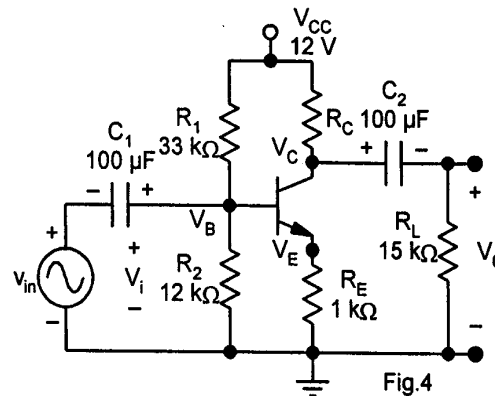**Table 1: Measured and calculated biasing conditions ($R_C = 3.3 \text{ k}\Omega$)**

Parameter	V_B	V_C	V_E	I_B	I_C	I_E	Mode
Calculated							
Measured							

- (v) Switch-off the +12V V_{CC} supply to the BJT circuit. Make $R_C=3.3 \text{ k}\Omega$. Now connect the electrolytic capacitors and R_L . Take care to observe the correct polarities when you connect the electrolytic capacitors.
- (vi) Adjust the FG output to give $0.2 \sin \omega t \text{ V}$ ($f=1 \text{ kHz}$). Switch on V_{CC} and connect the FG output to the BJT circuit through capacitor C_1 .
- (vii) Observe the amplifier input ($V_i = V_B$) and output V_O on CH-1 and CH-2, respectively.
- (viii) Sketch the two waveforms. Measure the voltage gain of the amplifier (Voltage gain, $A_V = V_O/V_i$).
- (ix) Comment on the phase relationship between the amplifier input and output waveforms.


Increasing the gain of the amplifier

In order to increase the gain, an engineer decided to increase value of R_C to $15 \text{ k}\Omega$.

- (i) Change R_C to $15 \text{ k}\Omega$.
- (ii) Measure the gain of the amplifier. Does it increase? If necessary, decrease the amplitude of the input signal.
- (iii) Measure the DC biasing conditions to determine the mode of operation of the BJT.

It is known from theory that the gain of the CE amplifier can be increased by connecting a capacitor in parallel with R_E .

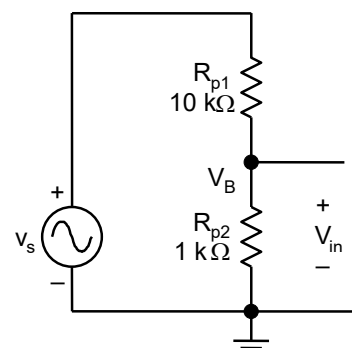- (i) Change R_C back to $3.3 \text{ k}\Omega$.
- (ii) Connect a $100 \mu\text{F}$ capacitor across R_E , and measure the gain. You may need to use a potential divider to reduce the amplitude of the input signal (5mV to 10mV peak) so that output signal waveform is undistorted.



Notes:

- $V_{\{XY\}} = V_X - V_Y$ where V_X is the voltage at node X
- measured with respect to ground
- B: base, E: emitter, C: collector
- $V_{\{BE\}} < 0.7$ V: transistor is cutoff
- $V_{\{BE\}} = 0.7$ V, $V_{\{CE\}} > 0.2$ V: transistor is in active region
- $V_{\{BE\}} = 0.7$ V, $V_{\{CE\}} = 0.2$ V: transistor is in saturation
- $I_C = \beta * I_B$ when the transistor is in active region.
- $I_E = (\beta + 1) * I_B$ when the transistor is in active region
- Take $\beta = 100$