

Name

OM SHIVASTAVA


Roll No.

210685


Seat/Room No.

362124

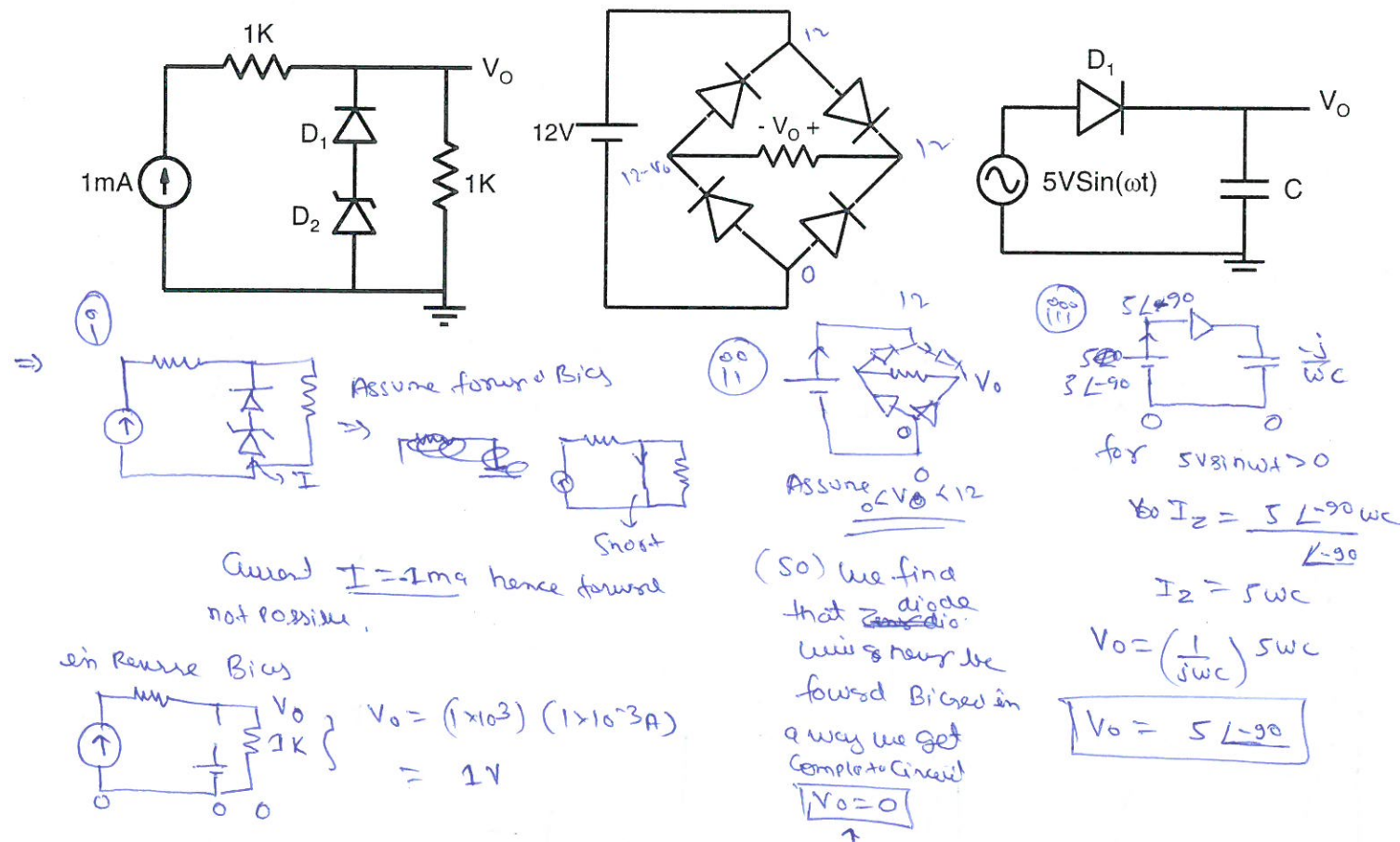1 (a). Determine the output voltage (steady state output in case of sinusoidal input) for the circuits shown below assuming that cut-in voltage of diode and Zener diode is 0V and that Zener voltage is 3V. Give proper reasoning for your answer. [4]



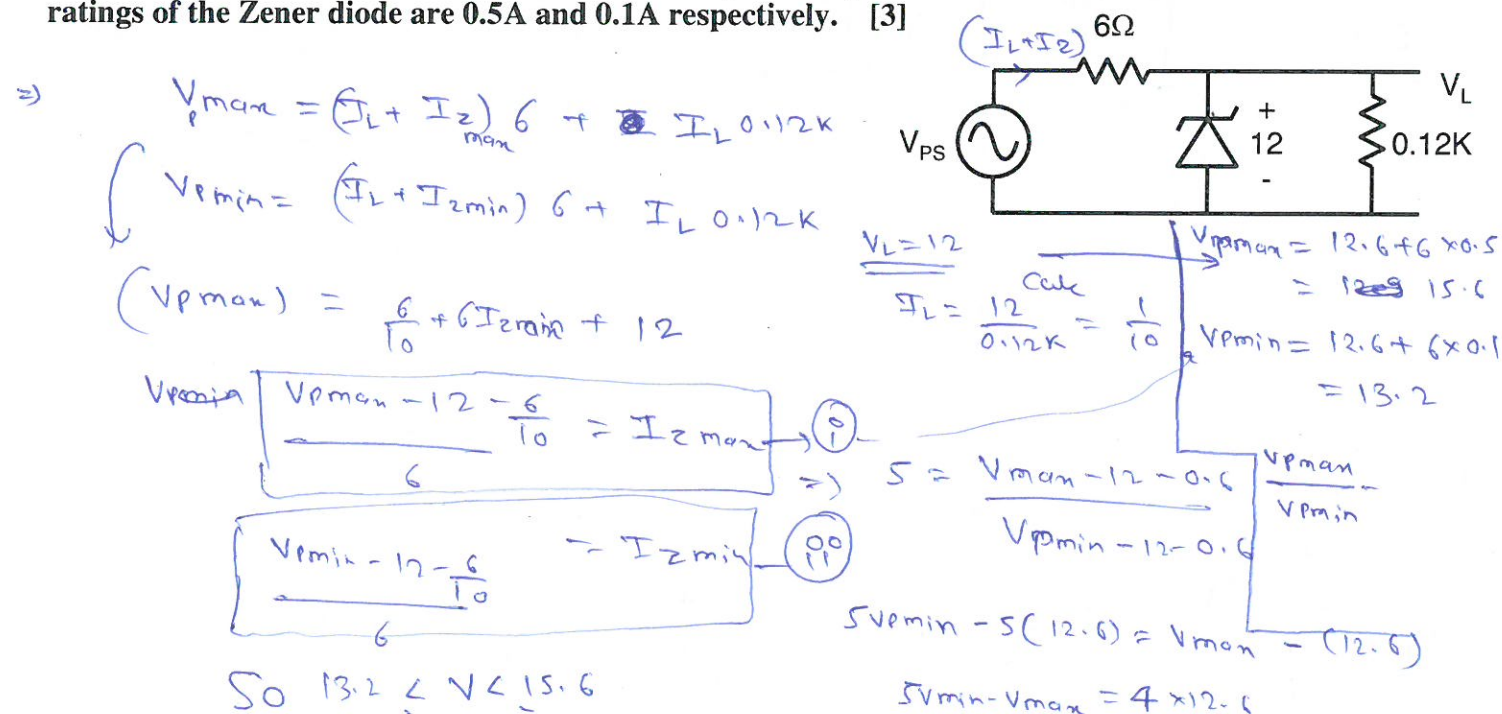1 (b). For the circuit shown below, determine the range of input voltage (minimum and maximum value) for which the circuit would provide a constant output voltage of 12V if the maximum and minimum current ratings of the Zener diode are 0.5A and 0.1A respectively. [3]



2(a). Obtain the transfer function $H(j\omega)$ corresponding to the Bode magnitude plot shown in the following figure. [4]

By the different segments given in

$$H(j\omega) = A \frac{(j\omega)^2}{\sqrt{1 + \left(\frac{\omega}{0.1}\right)^2} \sqrt{1 + \left(\frac{\omega}{1}\right)^2} \sqrt{1 + \left(\frac{\omega}{10}\right)^2} \sqrt{1 + \left(\frac{\omega}{100}\right)^2}}$$

$$= A \frac{(j\omega)^2}{(0.01)} \text{ At } \omega = 1$$

$$17 = 20 \log A + 20 \log(1) - 20 \log(10) - 20 \log(1) - 20 \log(1)$$

$$17 = 20 \log A - 20$$


$$\frac{37}{20} = \log A$$

$$A = 10^{37/20} = 70.794$$



$$H_{dB} = 20 \log \left(\frac{A(\omega)^2}{\sqrt{1 + \left(\frac{\omega}{0.1}\right)^2} \sqrt{1 + \left(\frac{\omega}{1}\right)^2} \sqrt{1 + \left(\frac{\omega}{10}\right)^2} \sqrt{1 + \left(\frac{\omega}{100}\right)^2}} \right)$$

$$\frac{17}{20} = \left(\frac{A}{10} \right)$$



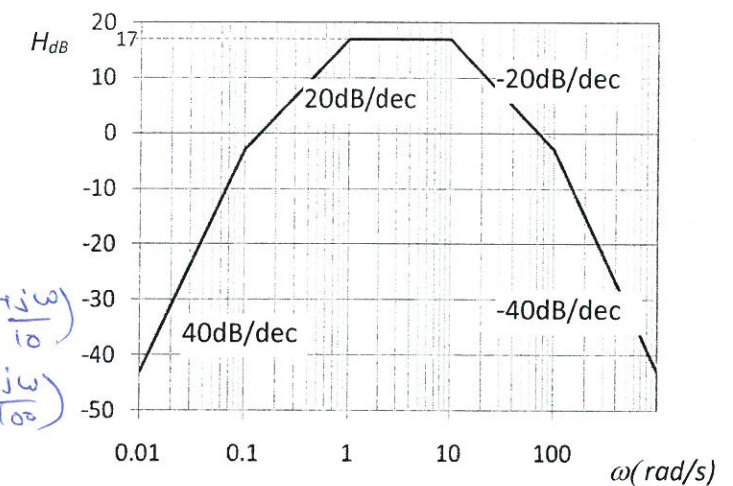
$$H(j\omega) = \frac{10(70.794)(j\omega)^2}{\left(1 + \frac{j\omega}{0.1}\right) \left(1 + \frac{j\omega}{1}\right) \left(1 + \frac{j\omega}{10}\right) \left(1 + \frac{j\omega}{100}\right)}$$



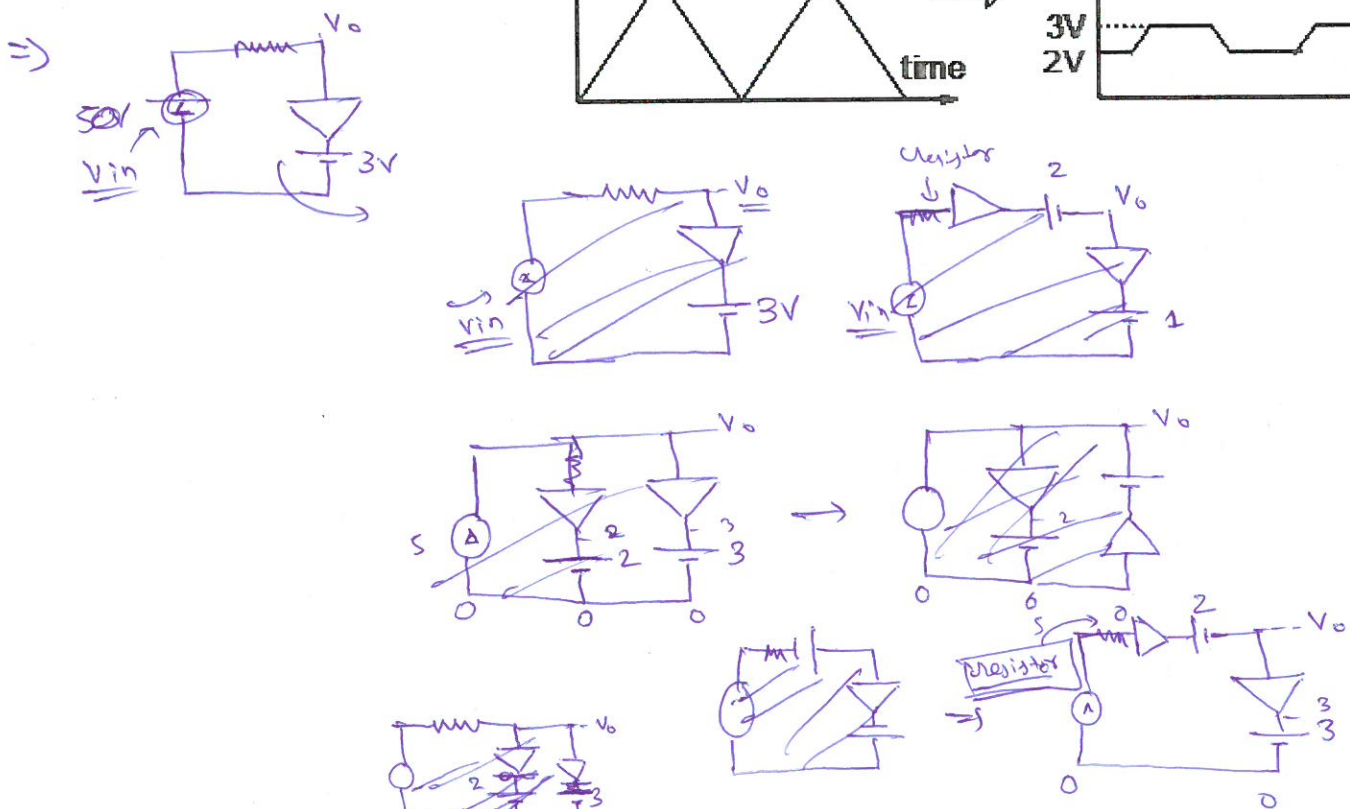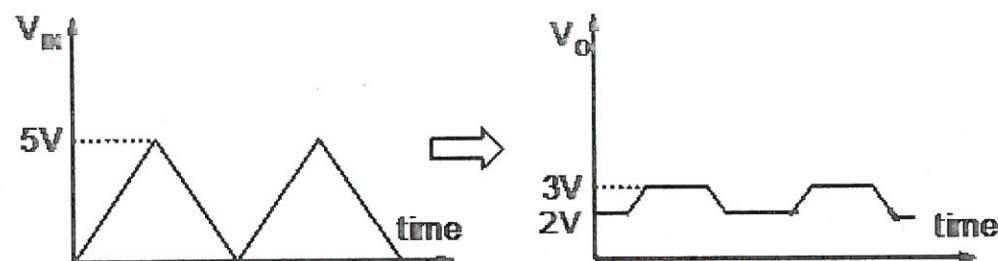2(b). Design a diode circuit to convert the triangular waveform into the waveform shown below. Give the circuit diagram along with typical component values. Assume ideal diodes with cut-in voltage of zero volts. [4]



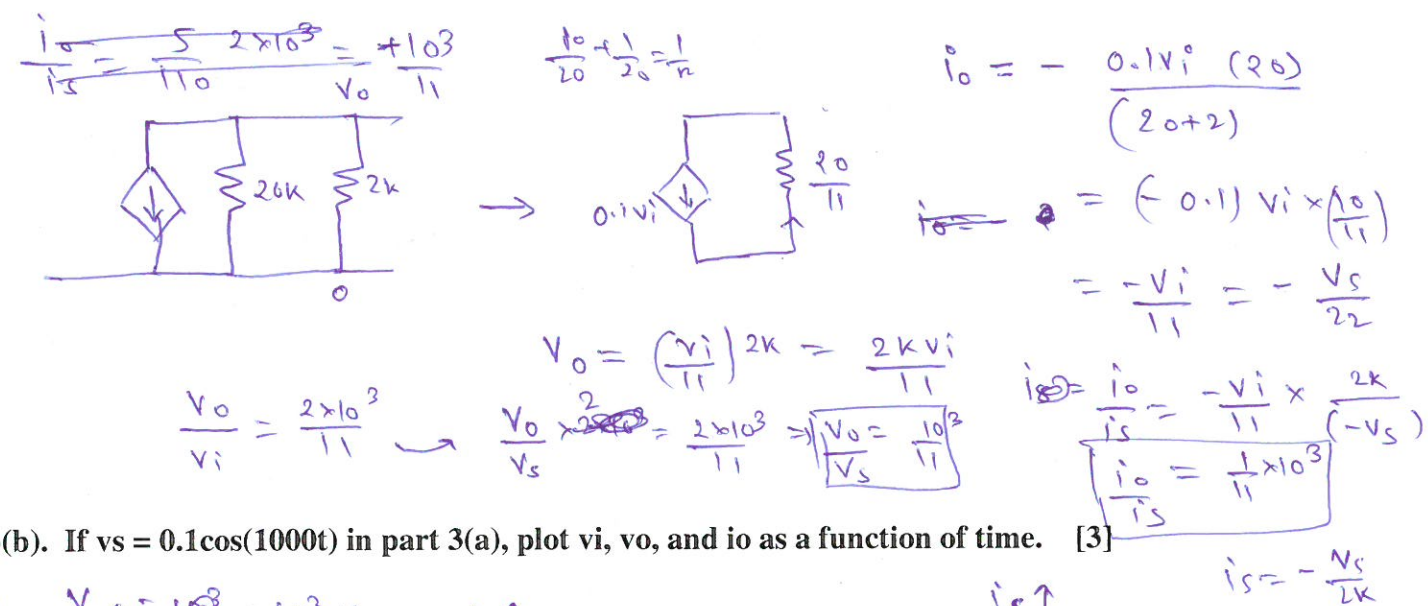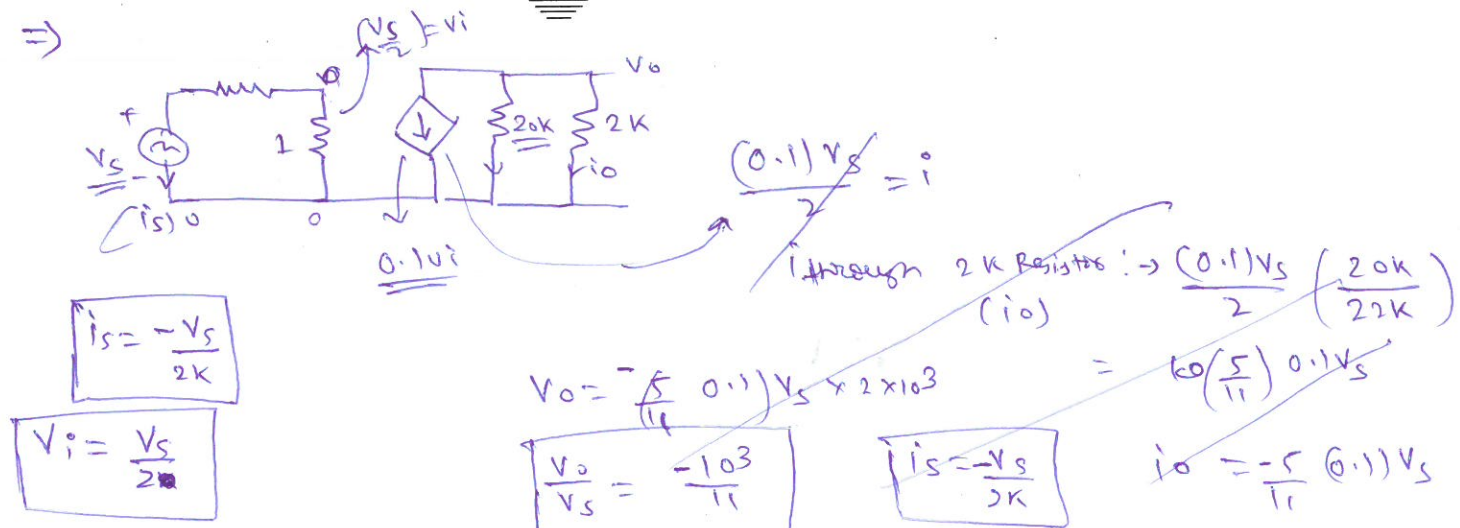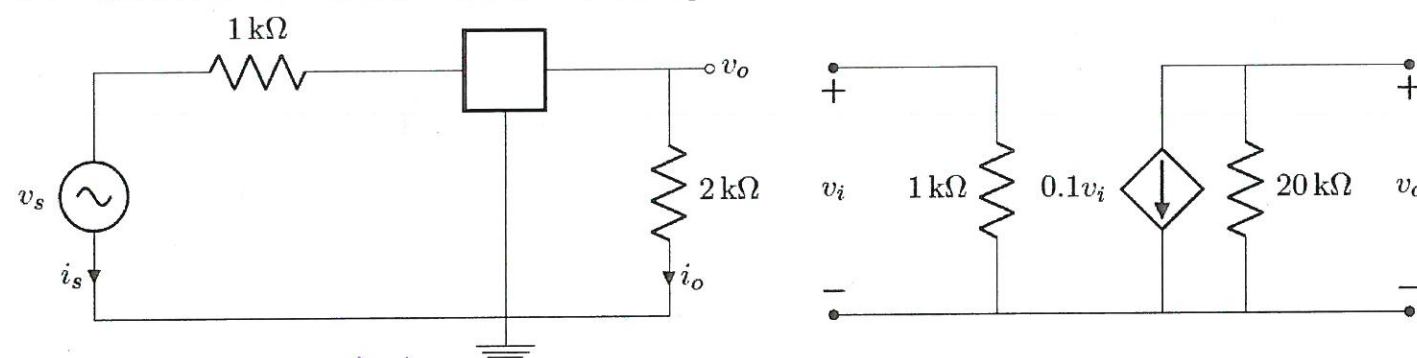3(a). Determine the voltage gain v_o/v_s and current gain i_o/i_s of the amplifier shown below on the left for the transistor model shown below on the right. [3]



3(b). If $v_s = 0.1\cos(1000t)$ in part 3(a), plot v_i , v_o , and i_o as a function of time. [3]

