

Name:	Roll. No.:	Section:	Duration: 55 mins Max. marks: 30 No. of questions: 2
-------	------------	----------	--

Mid-sem Exam - Part A

ESc201A

Write your answers here only.


Q 1. (a) N bulbs of resistance r each are connected in series in a straight line to form a setup of length L , driven by a DC supply. Our multimeter reads the currents and voltages at a rate 1000 samples per second. Which of the following assumptions need to be satisfied if we were to replace this setup of all the bulbs with a single resistance Nr ? (Mark \checkmark against them)

- ☒ There should be no charge leakage from the setup
- ☐ The charge leakage from the setup should be constant
- ☐ There should be no flux leakage from the setup
- ☒ The flux leaking from the setup should be constant
- ☒ The length L must be less than 300 km
- ☐ The length L must be less than 3 km


$$\begin{aligned}
 d &= c \times \tau \\
 &= c/f \\
 &= \frac{3 \times 10^8 \text{ m/s}}{1000 \text{ samples/s}} \\
 &= 3 \times 10^5 \text{ m} \\
 &= 300 \text{ km}
 \end{aligned}$$

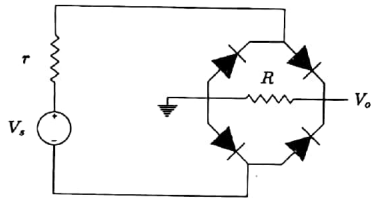Q 1. (b) Consider the following circuit. Assume constant voltage diode model ($V_f = 0.7 \text{ V}$, $r_D = 0$).

- Draw V_o (y-axis) vs V_s (x-axis, +ve and -ve). Mark all the points clearly. (5 marks)
- Write the expression for V_o in terms of given quantities and V_s . (5 marks)



When $V_s > 0$ & $i > 0$

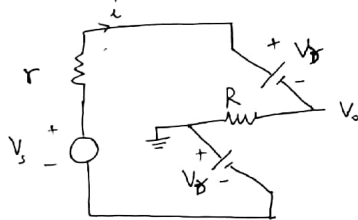

using KVL,

$$-V_s + ir + V_f + V_o + V_f = 0$$

Also, $i = V_o/R$

$$\therefore V_o + 2V_f + \frac{V_o r}{R} = V_s$$


$$V_o = \frac{V_s - 2V_f}{1 + \frac{r}{R}}$$

$$\begin{aligned}
 i &= \frac{V_o}{R} \text{ is } > 0 \text{ when} \\
 V_s - 2V_f &> 0 \\
 \Rightarrow V_s &> 2V_f
 \end{aligned}$$

When $V_s \in (0, 2V_f)$, then $i = 0$

$$\therefore V_o = iR = 0$$

When $V_s < 0$ & $i' > 0$

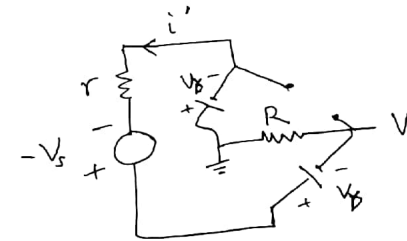

Using KVL,

$$\begin{aligned}
 -V_s - i'r - V_f - V_o - V_f &= 0 \\
 -V_s - i'R - 2V_f - V_o &= 0
 \end{aligned}$$


and $V_o = i'R$

$$V_o = \frac{-V_s - 2V_f}{1 + \frac{r}{R}}$$


$$\begin{aligned}
 i' &= \frac{V_o}{R} \text{ is } > 0 \text{ when} \\
 -V_s - 2V_f &> 0 \\
 \Rightarrow V_s &< -2V_f
 \end{aligned}$$

When $V_s \in (-2V_f, 0)$, then $i' = 0$


$$V_o = i'R = 0$$

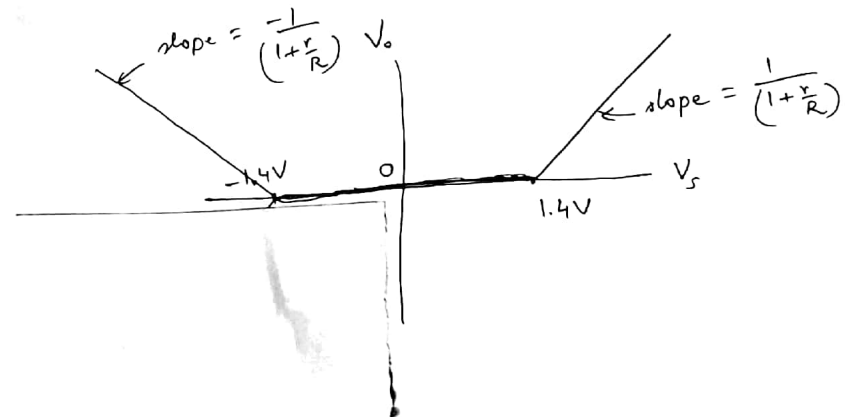

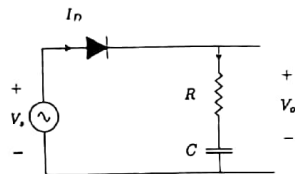Q 2. (a) In the single wave rectifier circuit, a student connected R in series with C, as shown below. Draw how will V_o look like with respect to time. (3 marks)



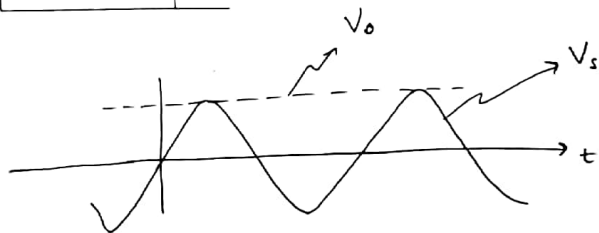
if someone draws V_o about R, we can give marks. It will be 0 V in steady state. No need to give or deduct marks for transient response.



C is charged and $I_D = 0$ always. C does not get discharged.

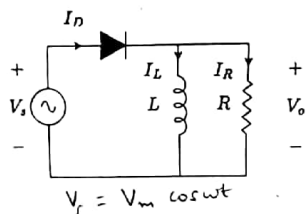Q 2. (b) In the single wave rectifier circuit, a student connected an inductor L instead of a capacitor. See figure below. Assume an ideal diode ($V_f = 0, r_D = 0$) to answer the following:

- Assuming the diode to be ON, plot the currents in the inductor, resistor and diode, as a function of time. (4 marks)
- Mark the time instance when the diode will turn OFF. (Hint: direction of diode current). Calculate this time instance. (4 marks)
- During the OFF state of the diode, plot the currents in the inductor, resistor and diode, as a function of time. (4 marks)



Assuming the diode is ON:-


i) $V_s = V_m \cos \omega t$

a) $L \frac{dI_L}{dt} = V_o = V_s = V_m \cos(\omega t) \Rightarrow I_L = \int \frac{V_m \cos \omega t}{L} dt$

b) $I_R R = V_o = V_s = V_m \cos(\omega t) \Rightarrow I_R = \frac{V_m \cos \omega t}{R}$

$\Rightarrow I_L = \frac{V_m \sin \omega t}{\omega L}$

c) $I_D = I_L + I_R$

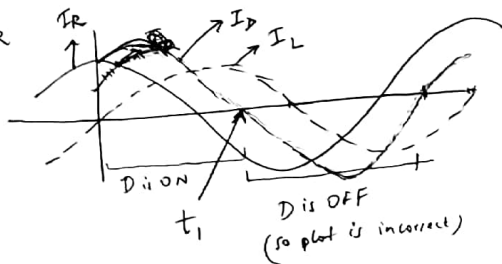

ii) t_1 is the time instance when the diode will turn OFF.

$$\frac{V_m}{R} \cos \omega t_1 \neq \frac{V_m}{\omega L} \sin \omega t_1 = 0 ; \omega t_1 \in \left(\frac{\pi}{2}, \pi\right)$$

$$\frac{\omega L \cos \omega t_1 + R \sin \omega t_1}{\sqrt{(\omega L)^2 + R^2}} = 0$$

$$\cos(\omega t_1 - \phi) = 0$$

$$\tan \phi = \frac{R}{\omega L}$$

$$\omega t_1 - \phi = \frac{\pi}{2}$$

$$\omega t_1 = \frac{\pi}{2} + \tan^{-1} \frac{R}{\omega L}$$

$$t_1 = \frac{1}{\omega} \left(\frac{\pi}{2} + \tan^{-1} \frac{R}{\omega L} \right)$$


iii) When Diode is off,



$$I_L + I_R = 0 \Rightarrow I_R = -I_L$$

and $I_L = I_{L,0} e^{-\frac{tR}{L}}$

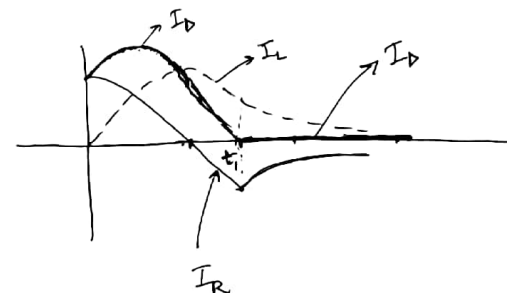here, $I_{L,0} = \frac{V_m}{\omega L} \sin(\omega t_1)$




Name:	Roll. No.:	Section:	Duration: 55 mins Max. marks: 30 No. of questions: 2
-------	------------	----------	--

Mid-sem Exam - Part B

ESc201A

Write your answers here only.

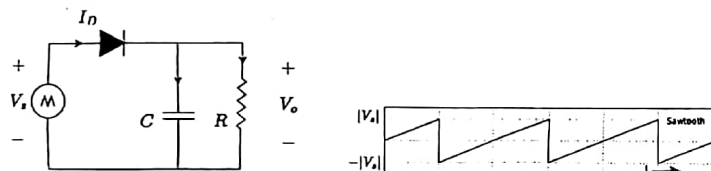
Q3. (a) In the single wave rectifier circuit, a student connected a sawtooth voltage source, instead of a sinusoidal one, as shown below. The frequency of source is f and the source voltage is plotted below. Assume a constant voltage diode model ($V_D = 0.7$ V, $r_D = 0$). Find the peak diode current. (5 marks)



$$V_o = V_s - 0.7 \text{ when } D \text{ is ON}$$

$$V_m = V_s - 0.7$$
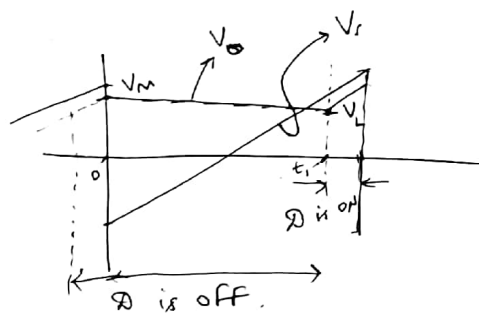
$$V_c = V_s - 0.7 \text{ when } D \text{ is ON}$$



$$I_D = C \frac{dV_o}{dt} + \frac{V_o}{R}$$


$$= C \frac{2|V_s|}{T} + \frac{V_o}{R}$$

$$\max I_D = \frac{2C|V_s|}{T} + \max \frac{V_o}{R} = \frac{2C|V_s|}{T} + \frac{V_m - 0.7}{R}$$

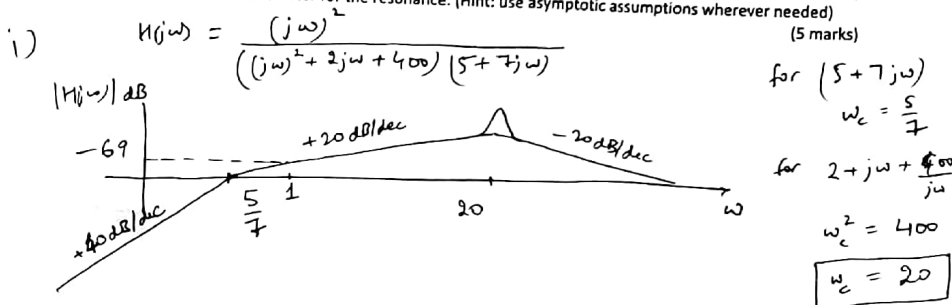Q3. (b) For the transfer function written below:

$$H(j\omega) = \frac{j\omega}{(2 + j\omega + \frac{400}{j\omega})(5 + 7j\omega)}$$

- Draw Bode magnitude plot (5 marks)
- Estimate the Q-factor for the resonance. (Hint: use asymptotic assumptions wherever needed) (5 marks)




$$\text{At } \omega = 1, \quad |H(j\omega)| = \frac{1}{400 \times 7}$$

$$20 \log |H(j\omega)| = -20 \log(2800) = -69$$

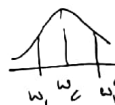ii) Q factor = $\frac{\omega_c}{\text{bandwidth}}$

To compute bandwidth:

$$\frac{1}{\sqrt{2^2 + (\omega_1 - \frac{400}{\omega_1})^2}} = \frac{1}{\sqrt{2}} \times \frac{1}{2} \text{ max. value (at } \omega_c)$$



$$(\omega_1 - \frac{400}{\omega_1})^2 = 2$$

$$\omega_1^2 \pm 2\omega_1 - 400 = 0$$


$$\Rightarrow \omega_1 = \frac{\pm 2 + \sqrt{4 + 4 \times 400}}{2}$$

(-ve sign ignored)
 $\therefore \omega_1, \omega_2 > 0$

$$\therefore \omega_2 - \omega_1 = \frac{2 \times 2}{2} = 2$$

$$\therefore Q = \frac{20}{2} = 10 \quad \text{Ans}$$

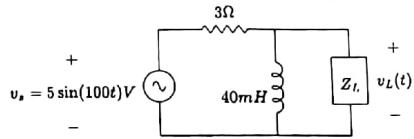Q 4. For the AC circuit shown below, voltage is given in terms of peak value.



- If $Z_L = 5 + 2j \Omega$, draw the phasor diagram showing V_s , I_s (current leaving the +ve terminal of voltage source), V_L and I_L (current entering the +ve terminal of Z_L). Mark the amplitude and phase of each quantity. (6 marks)
- If Z_L is variable, find the value of Z_L such that the reactive power supplied to the load has maximum magnitude. Also, write the value of reactive power. (Hint: use Thevenin's equivalent for easier calculations) (9 marks)

i) $V_s = 5 \angle -\frac{\pi}{2}$ V (rms)



$$I_s = \frac{5 \angle -\frac{\pi}{2}}{\sqrt{2} \angle -3.5j} = \frac{5 \angle -j}{\sqrt{2} \angle -3.5j}$$

$$= -0.35 - 0.63j \quad Z_{net} = 3 + (4j \parallel (5+2j)) = 3 + \frac{(4j)(5+2j)}{4j+5+2j}$$

$$= 0.7 \angle -120^\circ \text{ A (rms)} \quad = 3 + \frac{(-8+20j)}{(5+6j)} = 4.3 + 2.4j$$

$$V_L = V_s - 3I_s = 5 \angle -j + 3(0.35 + 0.63j) = 1.05 - 1.6j \text{ V (rms)} = 1.95 \angle -57^\circ$$
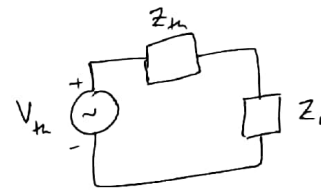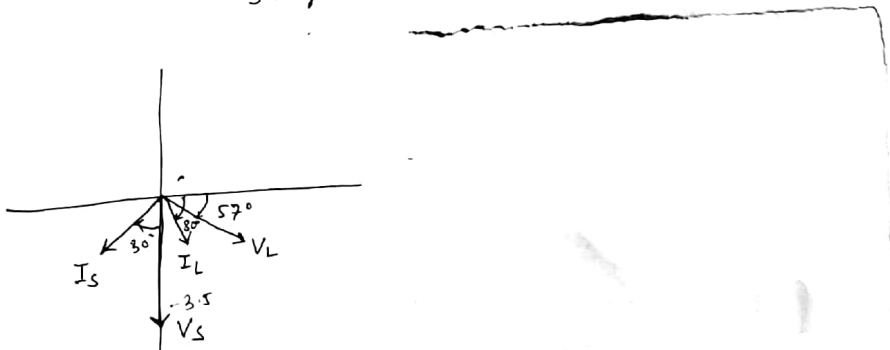
$$I_L = \frac{V_L}{5+2j} = \frac{1.05 - 1.6j}{5+2j} = 0.068 - 0.36j \text{ A (rms)} = 0.37 \angle -79^\circ$$



$$V_{th} = \frac{4j}{4j+3} \cdot 5 \angle -j = 1.7 - 2.3j = 2.8 \angle -53^\circ$$

$$(Let \ Z_L = R_L + jX_L) \quad Z_{th} = 3 \parallel 4j = 1.92 + 1.44j = 2.4 \angle 37^\circ$$

$$Q_L = \text{Im}(V_L I_L^*) = \text{Im}\left(V_L \frac{V_L^*}{Z_L^*}\right) = \text{Im}\left(\frac{|V_L|^2 Z_L}{|Z_L|^2}\right)$$

$$= \frac{|V_L|^2}{|Z_L|^2} X_L = |I_L|^2 X_L$$

$$= \frac{|V_{th}|^2}{|Z_{th} + Z_L|^2} X_L$$

$$= \frac{|V_{th}|^2 X_L}{(R_{th} + R_L)^2 + (X_{th} + X_L)^2}$$

$$\frac{\partial Q_L}{\partial R_L} = 0 \text{ gives -ve } R_L, \text{ which is not possible}$$

$$\therefore Q \text{ is min w.r.t. } R_L \text{ if } R_L = 0$$

$$\frac{\partial Q_L}{\partial X_L} = 0 \Rightarrow \frac{\partial}{\partial X_L} \left(\frac{X_L}{R_{th}^2 + (X_{th} + X_L)^2} \right) = 0$$

$$\Rightarrow R_{th}^2 + (X_{th} + X_L)^2 - X_L \cdot 2(X_{th} + X_L) = 0$$

$$R_{th}^2 + X_{th}^2 + X_L^2 + 2X_{th}X_L - 2X_{th}X_L - 2X_L^2 = 0$$

$$X_L^2 = X_{th}^2 + R_{th}^2$$

$$\therefore Z_L^* = |Z_{th}| j = 2.4j \Omega$$

$$Q_L \text{ at } Z_L^* =$$

$$\therefore X_L = \sqrt{R_{th}^2 + X_{th}^2} = |Z_{th}|$$

$$\frac{4(2.8)^2}{(4.3)^2} \times 2.4 = 1.02 \text{ VAR}$$